

Hendeca (11 Step) Resistance Substitution Box


This is an inexpensive way to make a stepped resistance box using a Single Pole - Twelve Position rotary switch and eleven resistors of equal value.

As there are eleven resistance steps for each rotary switch instead of the usual ten there is one step of overlap between switches.

The resistor tolerance can be 1, 5 or 10 percent, 5 percent is a good choice for most work. The wattage of the resistors depends on the maximum voltage that can be expected across a particular resistor. Lower resistances should be of higher wattage.

Two types of rotary switches are available, shorting and non-shorting. Either type will work but the non-shorting type will create a full switch cycle resistance circuit between each step. This may not be desirable in some applications.

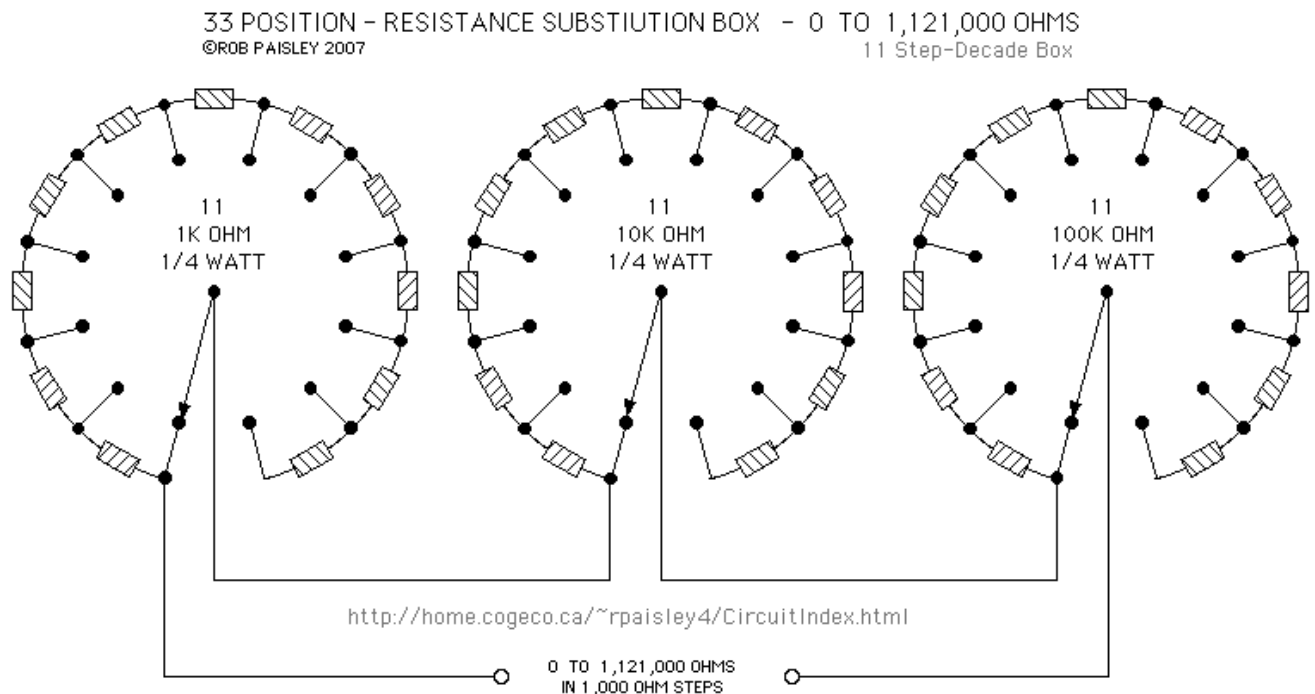33 Step - Hendeca Resistance Box Schematic



This is a photo of a 100 Ohm, twelve position switch. One-half watt resistors were used rather than one-quarter watt due to the expected higher current flow for these lower value resistors.

Switch Construction




Homemade Eleven Step Resistance Box




Two other substitution box possibilities.

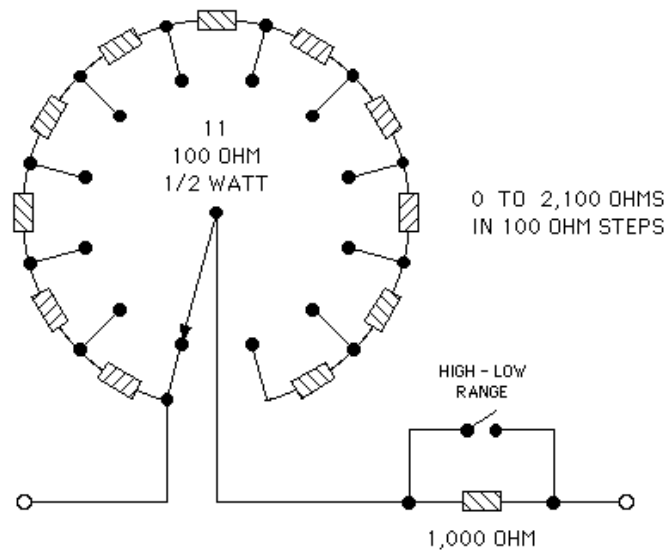11 POSITION - RESISTANCE SUBSTITUTION BOX - 0 TO 2,100 OHMS
 ©ROB PAISLEY 2007 11 Step Decade Box 2



<http://home.cogeco.ca/~rpaisley4/CircuitIndex.html>

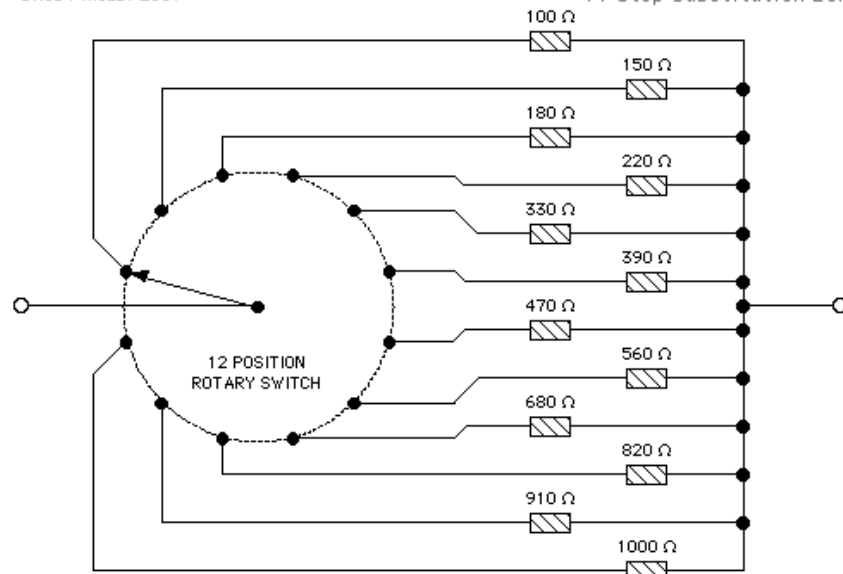12 POSITION - RESISTANCE SUBSTITUTION BOX - STANDARD VALUES
 ©ROB PAISLEY 2007 11 Step Substitution Box



<http://home.cogeco.ca/~rpaisley4/CircuitIndex.html>

5% Standard Values

Decade multiples are available from 10 Ω through 22 MΩ

10	11	12	13	15	16	18	20	22	24	27	30
33	36	39	43	47	51	56	62	68	75	82	91


10% Standard Values

Decade multiples are available from 10 Ω through 1 MΩ

10	12	15	18	22	27	33	39	47	56	68	82
----	----	----	----	----	----	----	----	----	----	----	----

Another possibility would be to connect a number of resistors of equal of various values in series on a terminal strip or perhaps a strip of wood with the resistors soldered to brass or copper nails. Different

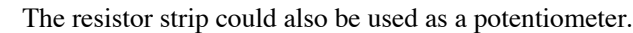Also, connecting the resistors in series instead of having individual resistors reduces the number of terminals needed from $2N$ to $N+1$ with 'N' being the number of resistors. (10 resistors in series = 11 terminals versus 20 terminals for separate resistors.)



The explanations for the circuits on these pages cannot hope to cover every situation on every layout. For this reason be prepared to do some experimenting to get the results you want. This is especially true of circuits such as the "Across Track Infrared Detection" circuits and any other circuit that relies on other than direct electronic inputs, such as switches.

Although the circuits are functional the pages are not meant to be full descriptions of each circuit but rather as guides for adapting them for use by others. If you have any questions or comments please send them to the email address on the [Circuit Index](#) page.

[Return to the Main Page](#)